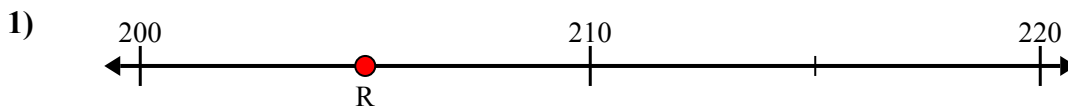





Найдите значение R.


Ответы




1. _____

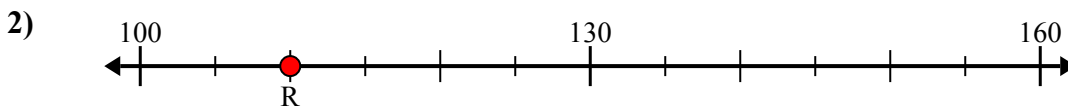


2. _____

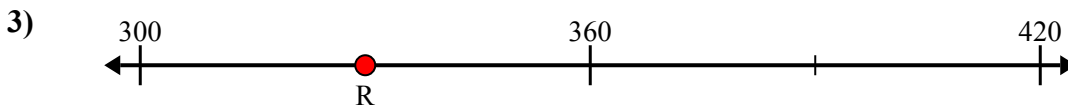


3. _____

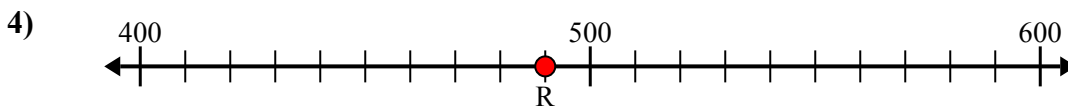


4. _____

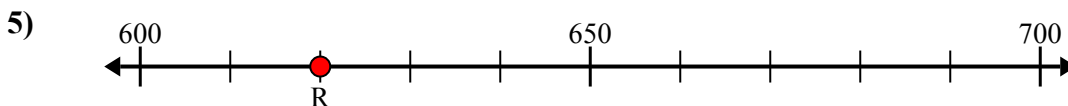


5. _____

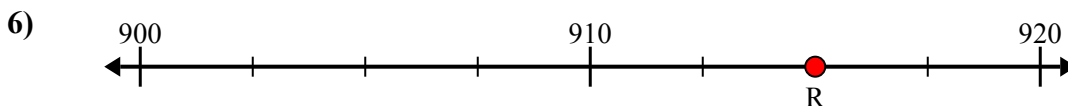


6. _____

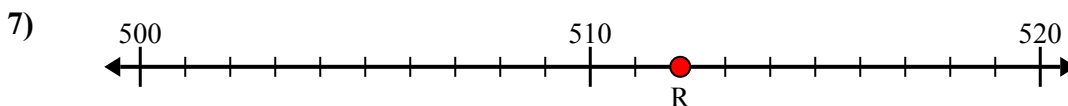


7. _____

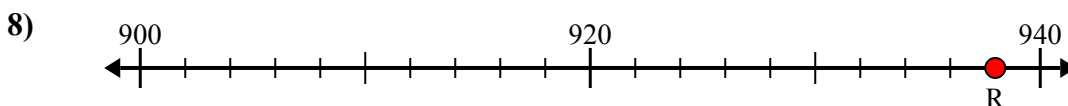

8. _____

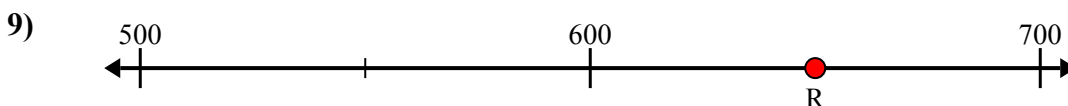

9. _____

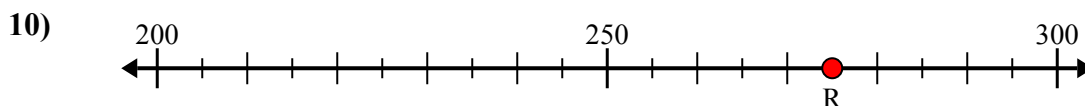


10. _____




Найдите значение R.


ОТВЕТЫ

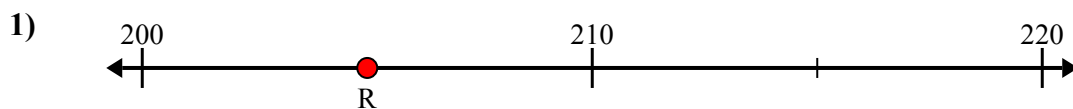

1. 205

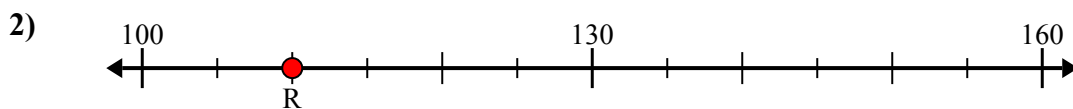


2. 110

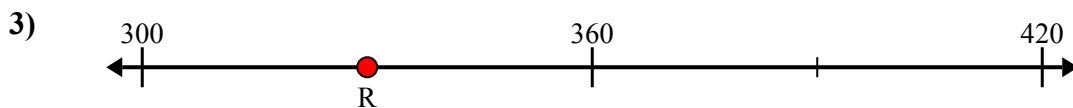


3. 330

4. 490

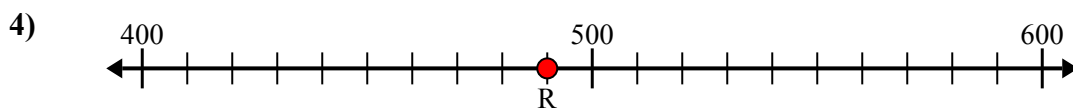


5. 620

6. 915

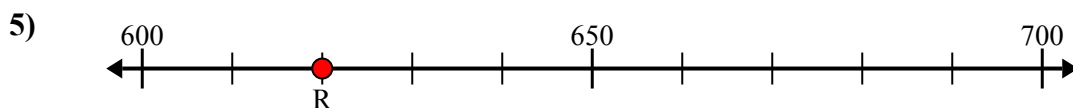

7. 512

8. 938

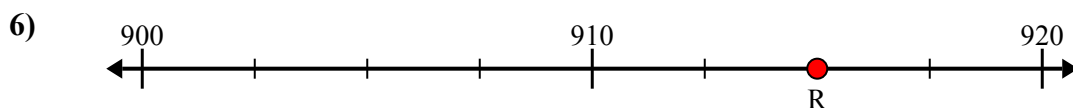

9. 650

10. 275

