

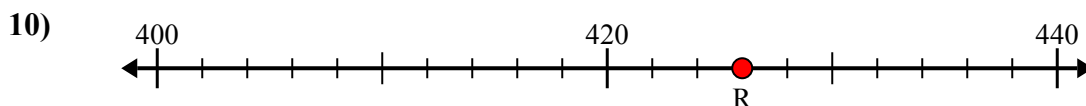
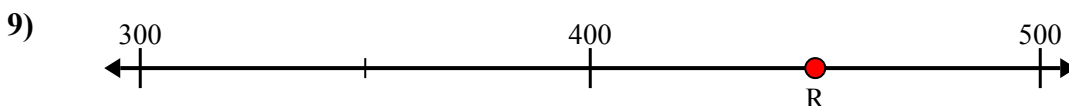
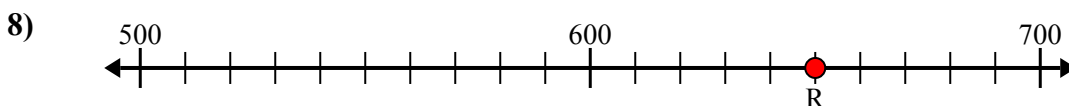
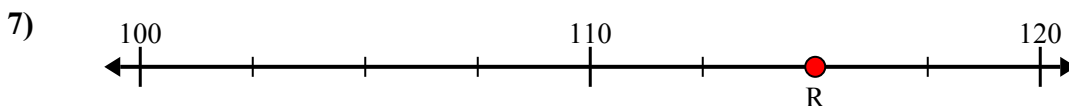
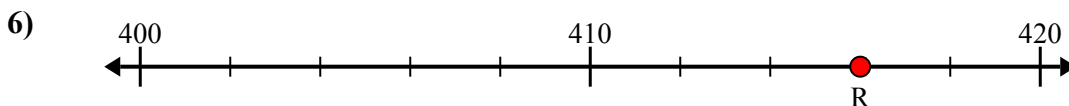
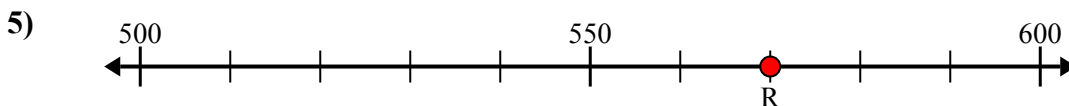
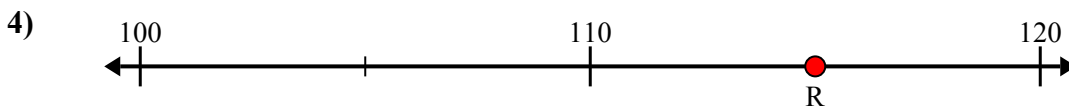
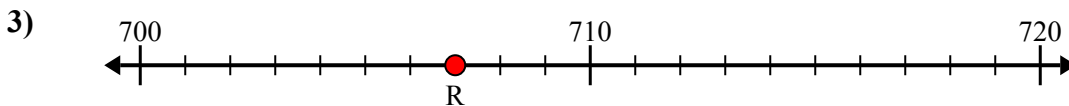


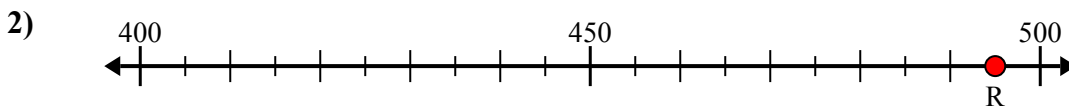

Найдите значение R.











Ответы

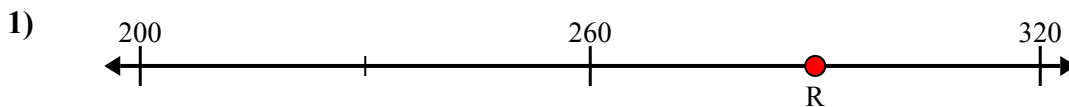

1. _____
2. _____
3. _____
4. _____
5. _____
6. _____
7. _____
8. _____
9. _____
10. _____



Найдите значение R.

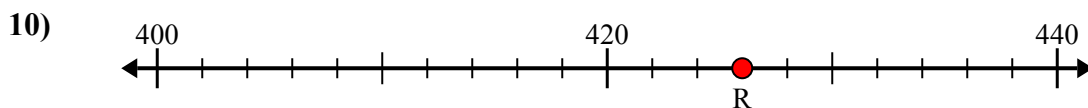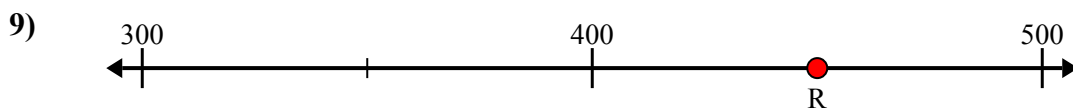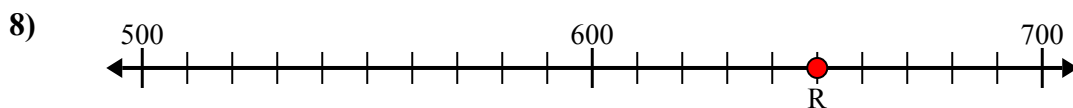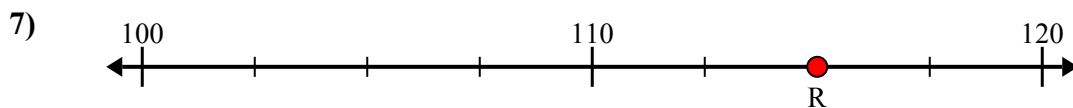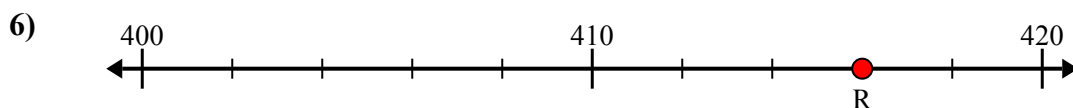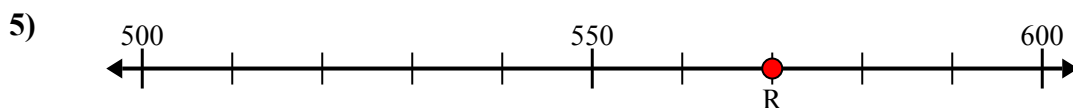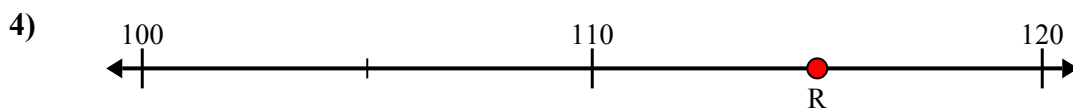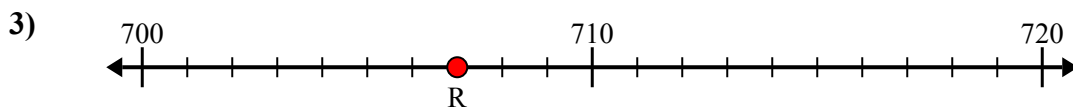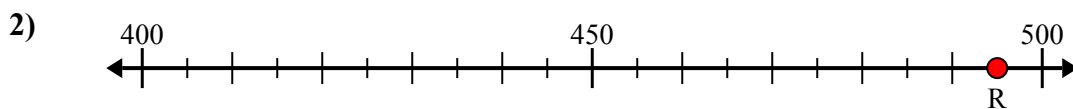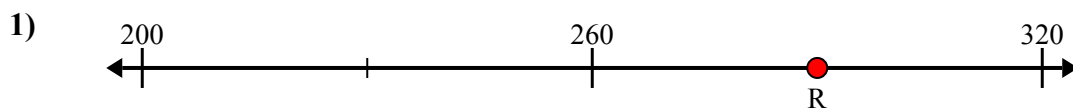

Ответы

1. 290

2. 495

3. 707

4. 115

5. 570

6. 416

7. 115

8. 650

9. 450

10. 426